

HY 232
Οργάνωση και
στον Σχεδίαση Η/Υ

Διάλεξη 8

Concepts of Digital Design
Introduction to Verilog

Νίκος Μπέλλας
Τμήμα Ηλεκτρολόγων και Μηχανικών Η/Υ

The Verilog Language


- A hardware description language (**HDL**) used for **modeling, simulation** and **synthesis** of digital electronic systems
- One of the two most commonly-used languages in digital hardware design (VHDL is the other)
- Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages
- Combines **structural** and **behavioral** modeling styles
- IEEE standard 1364-1995
- **Verilog-2001** extends the initial Verilog-95 specification

Simulation

- **Simulation** is used to verify the functional characteristics of models at any level of abstraction
- One of the main uses of Verilog/VHDL is simulation
- To test if the RTL code meets the functional requirements of the specification, we must see if all the RTL blocks are functionally correct.
- To achieve this we need to write a testbench, which generates *clk*, *reset* and the required test vectors
- Simulation is needed after every refinement step
 - Behavioral, zero-delay gate level, timing, post P&R simulation

How Are Simulators Used?

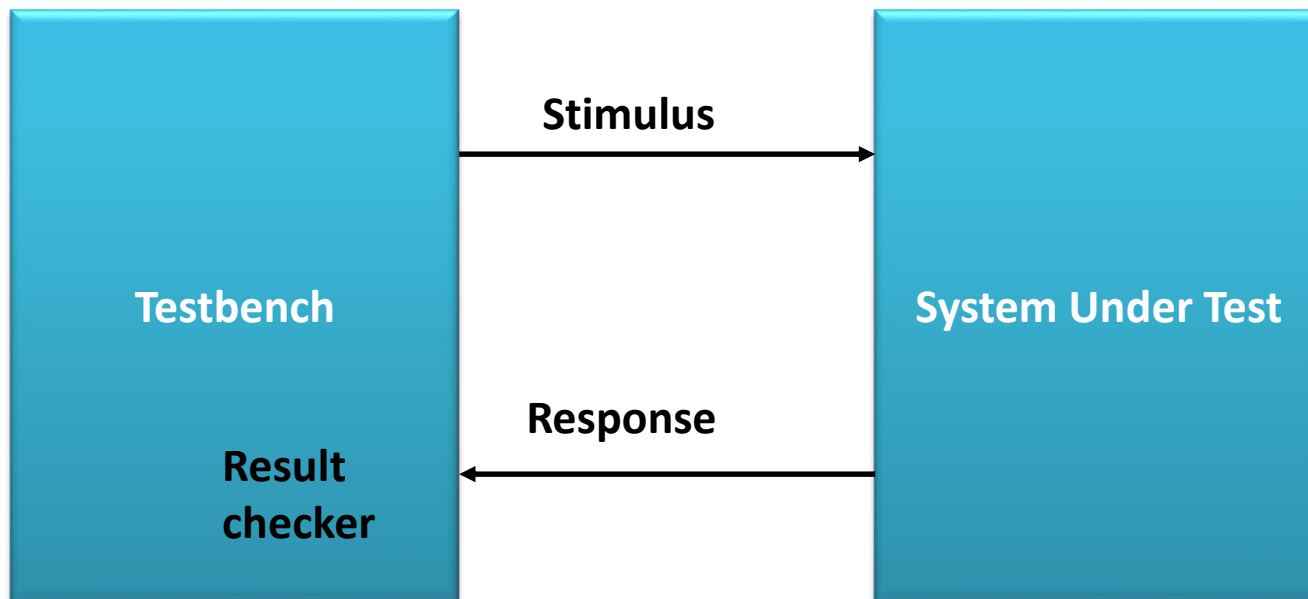- Testbench generates stimulus and checks response
- Coupled to model of the system
- Pair is run concurrently




Learn by Example: Combinational Logic

Adder: a circuit that does addition

Here's an example of binary addition:

Adding **TWO** N-bit numbers produces an (N+1)-bit result

```
  1101
+0101
-----
 10010
```

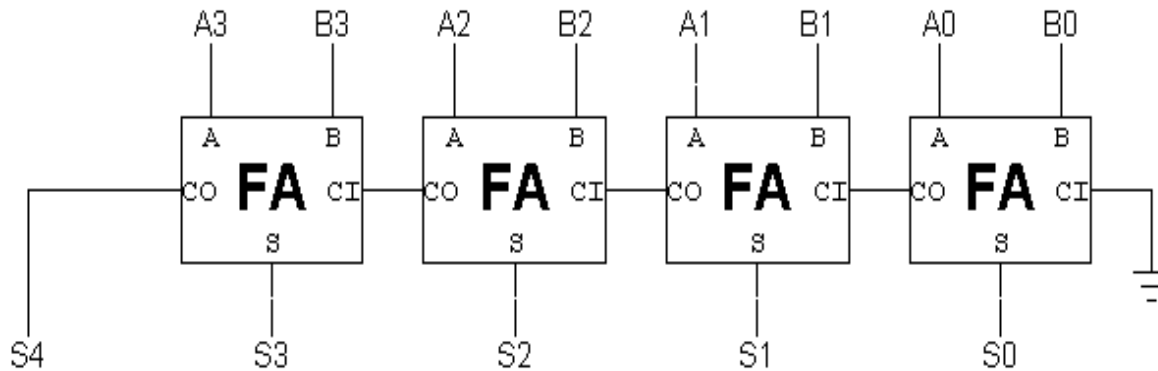

“Ripple-carry adder”

1-bit Adder

Build *Truth Table* and use *Sum of Products (SOP)*

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum: } S = A \oplus B \oplus C$$

Carry Out:

$$\begin{aligned} CO &= A'BC + AB'C + ABC' + ABC \\ &= (A' + A)BC + (B' + B)AC + AB(C' + C) \\ &= BC + AC + AB \end{aligned}$$

1-bit Adder

module: Basic unit of description

One line comment

// This is a behavioral module of 1-bit adder

module fulladd (Cin, x, y, s, Cout);

input Cin, x, y;

output s, Cout;

I/O ports with which the module communicates externally with other modules

assign s = x ^ y ^ Cin;

assign Cout = (x & y) | (x & Cin) | (y & Cin);

endmodule

Continuous assignment: the RHS is evaluated again every time the value of an operand changes. The LHS is assigned that value.

This is an example of **Behavioral Description**

4-bit Adder Structural Description

```
/* This is a structural module of 1-bit adder
*/
module adder4 (carryin, X, Y, S, carryout);
  input carryin;
  input [3:0] X, Y;
  output [3:0] S;
  output carryout;
  wire [3:1] C;

  fulladd stage0 (carryin, X[0], Y[0], S[0], C[1]);
  fulladd stage1 (C[1], X[1], Y[1], S[1], C[2]);
  fulladd stage2 (C[2], X[2], Y[2], S[2], C[3]);
  fulladd stage3 (C[3], X[3], Y[3], S[3], carryout);

endmodule
```

Multiple lines comment

Instantiation of the module *fulladd*

Arguments correspond to formal parameters of modules

Alternative N-bit Adder

```
module addern #(parameter n=32) (carryin, X, Y, S, carryout);
```

```
input carryin;
```

```
input [n-1:0] X, Y;
```

```
output [n-1:0] S;
```

```
output carryout;
```

```
reg [n-1:0] S;
```

```
reg carryout;
```

```
reg [n:0] C;
```

```
integer k;
```

```
always @(X, Y, carryin)
```

```
begin
```

```
    C[0] = carryin;
```

```
    for (k = 0; k < n; k = k+1)
```

```
    begin
```

```
        S[k] = X[k] ^ Y[k] ^ C[k];
```

```
        C[k+1] = (X[k] & Y[k]) | (X[k] & C[k]) | (Y[k] & C[k]);
```

```
    end
```

```
    carryout = C[n];
```

```
end
```

```
endmodule
```

n=32 sets default value for parameter n

reg is a data type that indicates a driver that can store a value.

If a signal is not **reg**, it is a **wire**

An **always** statement is only triggered at (@) the condition in the parenthesis (**sensitivity list**).

We execute the **always** statement only when X or Y or carryin change

Behavioral Description

Another one

```
module addern #(paramtere n=32) (carryin, X, Y, S, carryout, overflow);  
  input carryin;  
  input [n-1:0] X, Y;  
  output [n-1:0] S;  
  output carryout, overflow;  
  reg [n-1:0] S;  
  reg carryout, overflow;  
  
  always @(X or Y or carryin)  
  begin  
    S = X + Y + carryin;  
    carryout = (X[n-1] & Y[n-1]) | (X[n-1] & ~S[n-1]) | (Y[n-1] & ~S[n-1]);  
    overflow = carryout ^ X[n-1] ^ Y[n-1] ^ S[n-1];  
  end  
  
endmodule
```

S, X, Y are arrays

Behavioral Description

Language Elements and Expressions

Numbers in Verilog

- Integer numbers

- Simple decimal notation

- 32, -15

- Base format notation : *[size in bits]'base value*

- *Base* is one of d or D (decimal), o or O (octal), b or B (binary), h or H (hex). Use s for signed.

- 5'O37 // 5 bit octal number 37
- 4'D2 // 4 bit decimal number 2
- 4'B1x_01 // 4 bit binary number 1x01.
- 7'Hx // 7 bit hex xxxxxxx
- 8'shFF // Signed hex equal to -1
- 4'd-4 // Not legal. The sign is before the size.
- -4'd4 // 4-bit binary number -4. The sign is before the size
- (2+3)d'10 // Not legal. Size cannot be an expression

- The underscore character (`_`) is legal anywhere in a number except as the first character, where it is ignored

- When used in a number, the question mark (`?`) character is the Verilog alternative for the z character.

Numbers in Verilog

- Real numbers
 - Decimal notation
 - 32.0, -11.06
 - 2. // Not legal. Must have a digit on either side of decimal
 - Scientific notation
 - 23.51e2 // 2351.0
 - 23_5.1e1 // 2351.0
 - 5E-4

Strings in Verilog

- A string is a sequence of chars within double quotes
 - “Verilog is cool!”

Four-valued Data

- Verilog's nets and registers hold four-valued data
- 0, 1
 - Obvious
- Z (high impedance)
 - Output of an undriven tri-state driver
 - Models case where nothing is setting a wire's value
- X (unknown or undecided)
 - Models when the simulator can't decide the value
 - Initial state of registers
 - When a wire is being driven to 0 and 1 simultaneously
 - Output of a gate with Z inputs

Two Main Data Types

- **Wires** represent connections between things
 - Do not hold their value
 - Take their value from a driver such as a gate or other module
 - A signal is wire by default
- **Regs** represent data storage
 - Behave exactly like memory in a computer
 - Hold their value until explicitly assigned in an *initial* or *always* block
 - Can be used to model latches, flip-flops, etc., but do not correspond exactly
 - Shared variables with all their attendant problems

Nets and Registers

- Wires and registers can be bits, vectors, and arrays

```
wire a; // Simple wire
wire [15:0] dbus; // 16-bit bus
wire #(5,4,8) b; // Wire with rise delay 5, fall
    delay 4, and turn-off delay (hiZ) 8
reg [-1:4] vec; // Six-bit register
integer imem[0:1023]; // Array of 1024 integers
reg [31:0] dcache[0:63]; // A 32-bit mem with 64
    entries
```

Operators

- Arithmetic operators

- $X = (A+B)-C$ // binary plus and minus
- $X = -Y$ // unary minus
- $X = Y*Z$ // multiplication
- $X = A/B$ // division
- $X = A\%B$ // modulus is the remainder with
// the sign of the dividend.
// $7\%4 = 3$, $-7\%4 = -3$, $7\%-4 = 3$
- $X = A**B$ // exponent (Only in Verilog 2001)

Operators

- Relational operators
 - The result is 0 (false), 1 (true), or x (either operand has an x or z bit)
 - `23 > 45` // false (value 0)
 - `52 < 8'hxFF` // result is x
 - `'b1000 >= 'b01110` // false. Smaller sized operand is zero-filled

Operators

- Equality operators.

- `2'b10 == 4'b0010 // true`

- `'b11x0 == 'b11x0 // unknown because there is a bit in in either operand which is x (or z)`

- `'b11x0 === 'b11x0 // true. In case equality, x and z are compared strictly as values`

Operators

- Logical operators.
 - `A && B` // logical AND
 - `A || B` // logical OR
 - `!A` // logical NOT

Operators

- Bit-wise operators
 - $\sim A$ (unary negation)
 - $\&$ (binary and)
 - $|$ (binary or)
 - \wedge (binary xor)
 - $\sim \wedge$ (binary XNOR)

AND (&)

	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

OR (|)

	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

Operators

- Reduction operators
 - $A = 'b0110$, $B = 'b0100$, $C = 'b0x1$
 - $\&B$ is 0 // logical AND of all bits
 - $|B$ is 1 // logical OR of all bits
 - $\sim\&A$ is 1 // logical NAND of all bits
 - $\wedge B$ is 1 // logical XOR of all bits
 - $\sim\wedge B$ is 0 // logical XNOR of all bits
 - $\&C$ is 0 // at least a bit is 0
 - $|C$ is 1 // at least a bit is 1
 - $\wedge C$ is x // if any bit is x or z, result is x

Operators

- Shift operators
 - $A \gg B$ // logical right shift
 - $A \ll B$ // logical left shift
 - $A \ggg B$ // right shift for signed numbers (Only Verilog 2001)
 - $A \lll B$ // left shift for signed numbers (Only Verilog 2001)
- Conditional operator
 - $\text{cond_expr? expr1 : expr2}$

Operators

- Concatenation and Replication operators
 - `wire [7:0] Dbus`
 - `wire [11:0] Abus`
 - `assign Dbus = {Dbus[3:0], Dbus[7:4]} //`
`concatenation: swap nibbles`
 - `Abus = {3{4'b1011}} // 12'b1011_1011_1011`

**Two ways to express hardware in
Verilog:
Structural and Behavioral Models**

Two Main Components of Verilog

- Concurrent, event-triggered processes (behavioral)
 - *Initial* and *Always* blocks
 - Imperative code that can perform standard data manipulation tasks (assignment, if-then, case)
 - Processes run until they delay for a period of time or wait for a triggering event
- Structure (structural)
 - Verilog program built from modules with I/O interfaces
 - Modules may contain instances of other modules
 - Modules contain local signals, etc.
 - Module configuration is static and all run concurrently
- High level modules typically structural
- Low level modules (leaves) typically behavioral

Structural Modeling

- When Verilog was first developed (1984) most logic simulators operated on netlists
- Netlist: list of gates and how they're connected
- A natural representation of a digital logic circuit
- **Not** the most convenient way to express test benches

Behavioral Modeling

- A much easier way to write testbenches
- Also good for more abstract models of circuits
 - Easier to write
 - Simulates faster
- More flexible
- Provides sequencing
- Verilog succeeded in part because it allowed both the model and the testbench to be described together

Multiplexer Built From Primitives

```
module mux(f, a, b, sel);  
  output f;  
  input a, b, sel;
```


Identifiers not explicitly defined default to wires

Module may contain structure: instances of primitives and other modules

Predefined module types

```
  and g1(f1, a, nsel),  
    g2(f2, b, sel);  
  or g3(f, f1, f2);  
  not g4(nsel, sel);
```

```
endmodule
```

 


Multiplexer Built With Always

```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
reg f;
```

```
always @(a, b, sel)  
  if (sel)  
    f = b;  
  else  
    f = a;  
endmodule
```

Modules may contain one or more *always* blocks


 
Sensitivity list contains signals whose change triggers the execution of the block



Mux with Continuous Assignment

```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
  
assign f = sel ? b : a;  
  
endmodule
```

 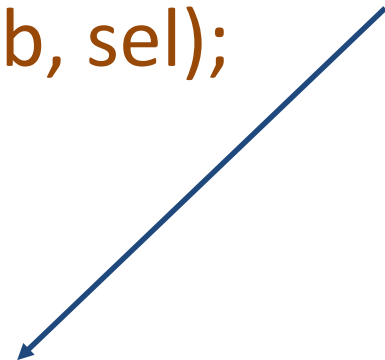LHS is always set to the value on the RHS
Any change on the right causes reevaluation




Structural Modeling in more detail

Modules and Instances

- Basic structure of a Verilog module:

```
module mymod(port1, port2, ... portN);  
  output port1;  
  output [3:0] port2;  
  input [2:0] portN;  
  ...  
endmodule
```



Verilog convention lists outputs first. This is not necessary

Modules and Instances

- Verilog 2001 allows port direction and data type in the port list of modules as shown in the example below

```
module mymod(output port1,  
             output [3:0] port2,  
             ...  
             input [2:0] portN);  
  
...  
endmodule
```

Instantiating a Module

- Instances of

```
module mymod(y, a, b);
```

- look like

```
mymod mm1(y1, a1, b1);           // Connect-by-position  
mymod (y2, a1, b1),  
      (y3, a2, b2);             // Instance names omitted  
mymod mm2(.a(a2), .b(b2), .y(c2)); // Connect-by-name
```

Gate-level Primitives

- Verilog provides the following keywords for gate level modeling:

and	nand	logical AND/NAND
or	nor	logical OR/NOR
xor	xnor	logical XOR/XNOR
buf	not	buffer/inverter
bufif0	notif0	Tristate buf with low enable
bifif1	notif1	Tristate buf with high enable

Switch-level Primitives

- Verilog also provides mechanisms for modeling CMOS transistors that behave like switches
- A more detailed modeling scheme that can catch some additional electrical problems when transistors are used in this way
- Rarely used because circuits generally aren't built this way
- More seriously, model is not detailed enough to catch many of the problems
- These circuits are usually simulated using SPICE-like simulators based on nonlinear differential equation solvers

Behavioral Modeling in more detail

Types of Assignments in Verilog

- **Continuous** and **Procedural** Assignments
- **Continuous assignments** model combinational behavior only
 - They assign a value to a wire (never to a reg)
 - *assign LHS_target = RHS_expression*
 - The continuous statement executes every time an event happens in the RHS expression
 - The expression is evaluated
 - If the result is different, the new value is assigned to the LHS target

Continuous Assignment

- Convenient for logical or data path specifications

Define bus widths

wire [8:0] sum;

wire [7:0] a, b;

wire carryin;

assign sum = a + b + carryin;

Continuous assignment:
permanently sets the value
of sum to be a+b+carryin
Recomputed when a, b, or
carryin changes

Types of Assignments in Verilog

- **Procedural assignments** model combinational and sequential behavior
- They appear only within an **initial statement** or an **always statement**
- Two different types of procedural assignments
 - Blocking
 - Non-blocking

Initial and Always Blocks

- Basic components for behavioral modeling

initial

begin

... imperative statements ...

end

Runs when simulation starts

Terminates when control reaches the end

Good for providing stimulus in testbenches

always

begin

... imperative statements ...

end

Runs when simulation starts

Restarts when control reaches the end

Good for modeling/specifying hardware

Timing Controls

- Two forms of timing control:
 - Delay control
 - Event control

Delay Controls

- **Delay** control is of the form

delay <procedural statement>

It specifies the time units from the time the statement is initially encountered to the time it is executed

e.g.

#2 input = 4'b0101; // wait for 2 units, and then make
the assignment

input = #1 x // assign to *input* the value that *x* will have after
1 time unit. Different than **#1 input = x**

Event Controls

- **Edge-triggered** event control is of the form

@ event <procedural statement>

e.g. @ (posedge clk) curr_state = next_state

@ (X or Y) A <= 0; // when X or Y change

- **Level-triggered** event control is of the form

wait (condition) <procedural statement>

The statement executes only if the condition is true, else it waits until the condition becomes true.

e.g. wait(DataReady);

Data = Bus

Initial and Always

- Run until they encounter a delay

```
initial begin
    #10 a = 1; b = 0;
    #10 a = 0; b = 1;
end
```

- or a wait for an event

```
always @(posedge clk) q = d;
always
    begin
        wait(i); a = 0; wait(~i); a = 1;
    end
```

Blocking Procedural Assignment

- Inside an initial or always block:

```
sum = a + b + cin;
```

- Just like in C: RHS evaluated and assigned to LHS before next statement executes
- RHS may contain wires and regs
 - Two possible sources for data
- LHS must be a reg
 - Primitives or cont. assignment may set wire values

Imperative Statements

```
if (select == 1)    y = a;  
else                y = b;
```

```
case (op)  
  2'b00: y = a + b;  
  2'b01: y = a - b;  
  2'b10: y = a ^ b;  
  default: y = 'hxxxx;  
endcase
```

For Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
for ( i = 0 ; i <= 15 ; i = i + 1 ) begin
```

```
    output = i;
```

```
    #10;
```

```
end
```

While Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
i = 0;
```

```
while (i <= 15) begin
```

```
    output = i;
```

```
    #10 i = i + 1;
```

```
end
```

Blocking vs. Non Blocking Assignments

- Verilog has two types of procedural assignments
- Fundamental problem:
 - In a synchronous system, all flip-flops sample simultaneously
 - In Verilog, always @(posedge clk) blocks run in some undefined sequence

A Flawed Shift Register

- This doesn't work as you expect:

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 = d1;
```

```
always @(posedge clk) d3 = d2;
```

```
always @(posedge clk) d4 = d3;
```

- These run in some order, but you don't know which

Non-blocking Assignments

- This version does work:


```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 <= d1;
```


```
always @(posedge clk) d3 <= d2;
```

```
always @(posedge clk) d4 <= d3;
```

Nonblocking rule:
RHS evaluated when
assignment runs



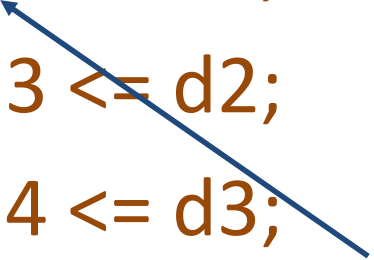LHS updated only after all
events for the current instant
have run. It runs after a *Delta*



Nonblocking Can Behave Oddly

- A sequence of nonblocking assignments don't communicate

```
a = 1;  
b = a;  
c = b;
```

```
Blocking assignment:  
a = b = c = 1
```

```
a <= 1;  
b <= a;  
c <= b;
```


Nonblocking assignment after δ time:

```
a = 1  
b = old value of a  
c = old value of b
```


Nonblocking Looks Like Latches

- RHS of nonblocking taken from latches
- RHS of blocking taken from wires

`a = 1;`
`b = a;`
`c = b;`

 


`a <= 1;`
`b <= a;`
`c <= b;`

 

Sequential Logic and Finite State Machines in Verilog

Why we need sequential logic?

 What if you were given the following design specification:




What makes this circuit different from those we've discussed before?

1. "State" – i.e. the circuit has memory
2. The output was changed by a input "event" (pushing a button) rather than an input "value"

Digital State

One model of what we'd like to build

 



Plan: Build a Sequential Circuit with stored digital STATE –

- Memory stores CURRENT state
- Combinational Logic computes
 - NEXT state (from input, current state)
 - OUTPUT bit (from input, current state)
- State changes on LOAD control input



If Output depends on Input and current state, circuit is called a **Mealy** machine.
If Output depends only on the current state, circuit is called a **Moore** machine.

Our building block: the D FF

  The edge-triggered D register: on the rising edge of CLK, the value of D is saved in the register and then shortly afterwards appears on Q.



D-Register Timing

  


t_{PD} : maximum propagation delay, CLK \rightarrow Q

t_{CD} : minimum contamination delay, CLK \rightarrow Q

t_{SETUP} : setup time
How long D must be stable before the rising edge of CLK

t_{HOLD} : hold time
How long D must be stable after the rising edge of CLK

The Sequential always Block

 

```

module dff (input D, CLK, output reg Q);
always @(posedge clk)
begin
    Q<=D;
end
endmodule;
    
```



```

module CL(input a,b, sel,
           output reg out);
always @(*)
begin
    if (sel) out = b;
    else out = a;
end
endmodule;
    
```



```

 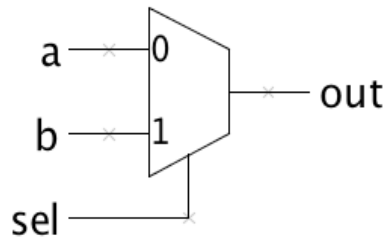
module SL(input a,b, sel,
           output reg out);
always @(posedge clk)
begin
    if (sel) out <= b;
    else out <= a;
end
endmodule;
    
```



Finite State Machines and Verilog

Finite State Machines

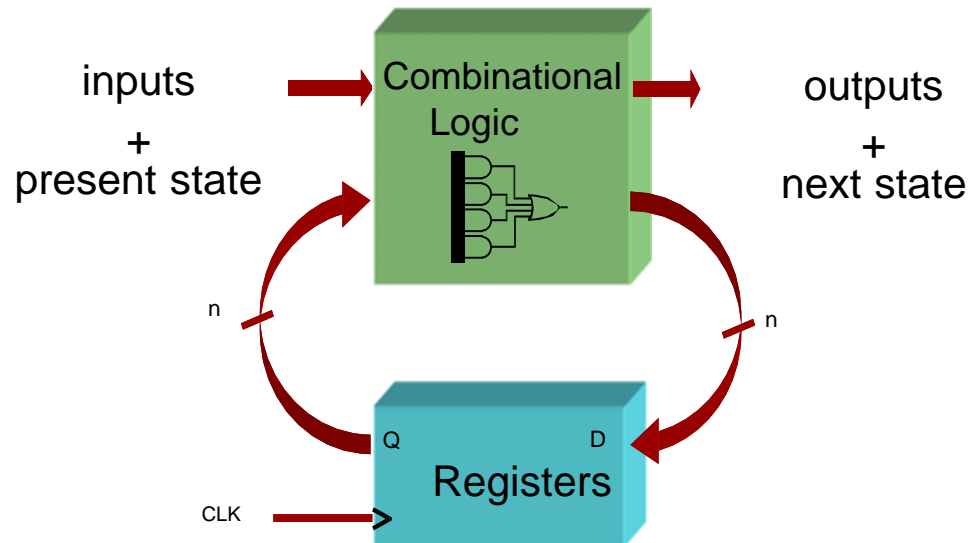
- Finite State Machines (FSMs) are a useful abstraction for sequential circuits with centralized “states” of operation
- At each clock edge, combinational logic computes outputs and next state as a function of inputs and present state




Two types of Finite State Machines

Moore and Mealy FSMs : different output generation

• Moore FSM:

 


• Mealy FSM:

 

Design Example: Level-to-Pulse

 
- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters



Step 1: State Transition Diagram




 - **State transition diagram** is a useful FSM representation and design aid:




Step 2: Logic Derivation

 Transition diagram is readily converted to a state transition table (just a truth table)




Current State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

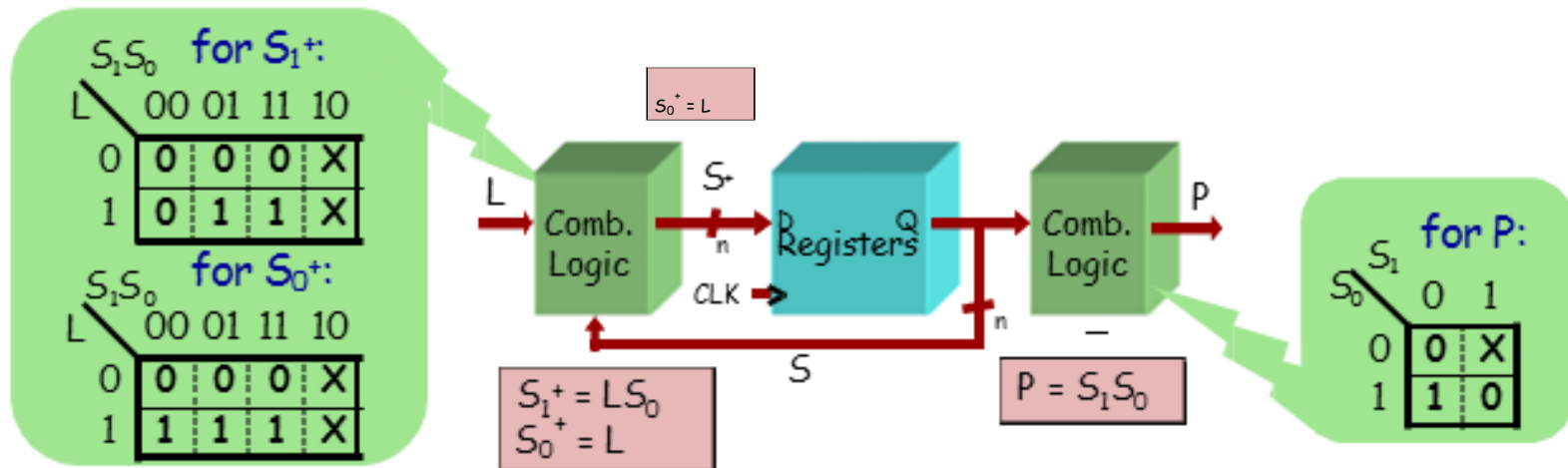
- Combinational logic may be derived using Karnaugh maps




Moore Level-to-Pulse Converter

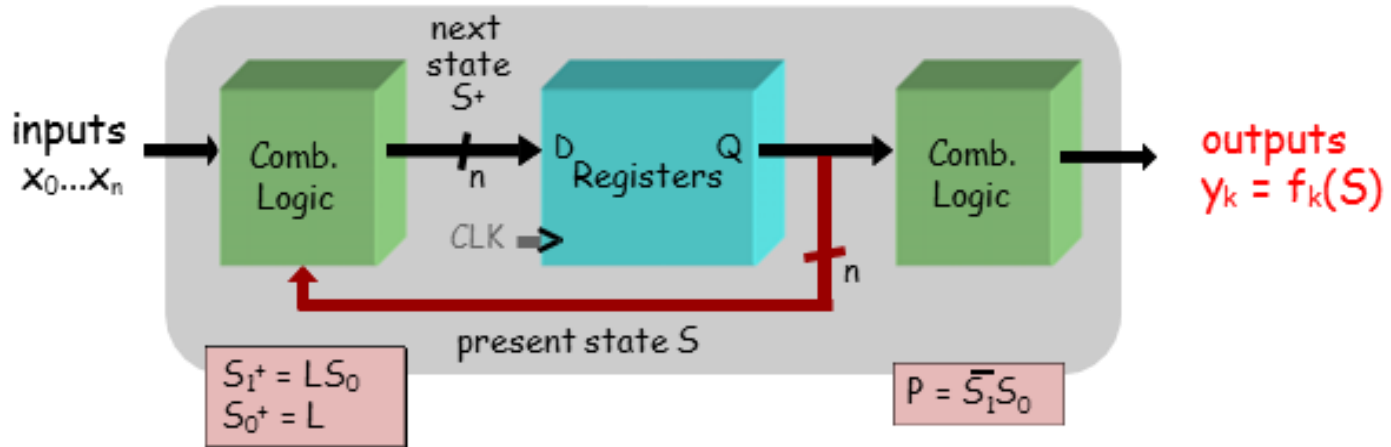

 
Moore FSM circuit implementation of level-to-pulse converter:




Design of a Mealy Level-to-Pulse

 

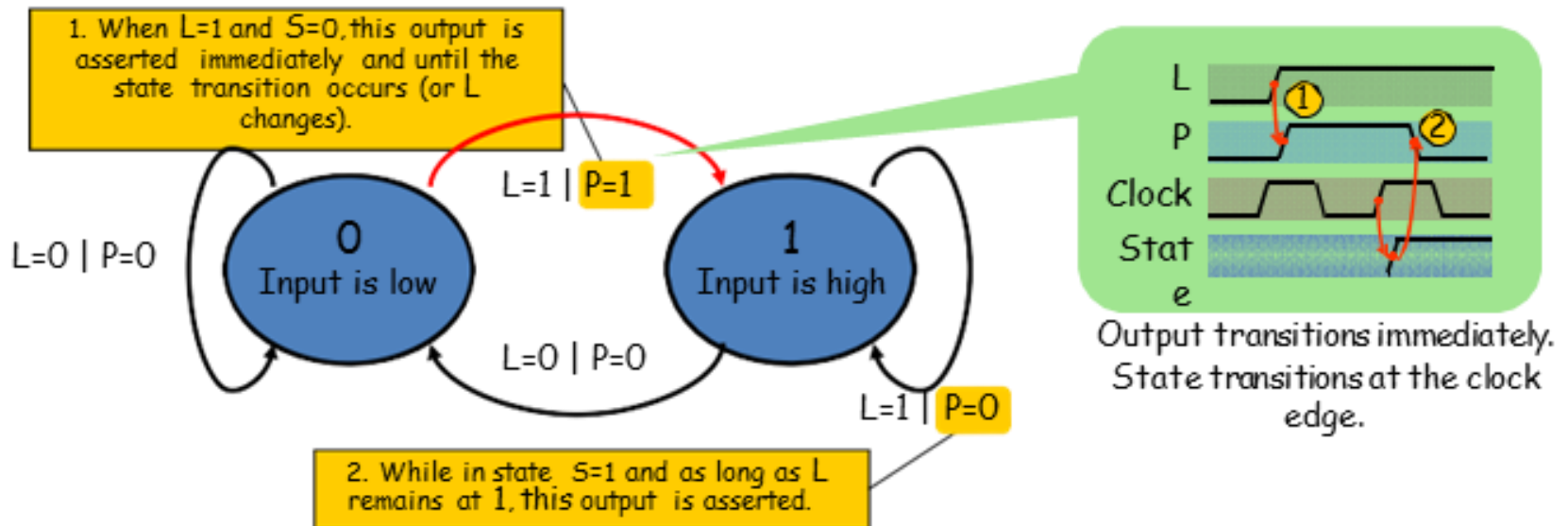- Since outputs are determined by state and inputs, Mealy FSMs may need fewer states than Moore FSM implementations




Design of a Mealy Level-to-Pulse

 

Pres. State	In	Next State	Out
S	L	S+	P
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

 Mealy FSM circuit implementation of level-to-pulse converter:



- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions

Second FSM Example

GOAL:


Build an electronic combination lock with a reset button, two number buttons (0 and 1), and an unlock output. The combination should be **01011**.




STEPS:

1. Design lock FSM (block diagram, state transitions)
2. Write Verilog module(s) for FSM

Step 1A: Block Diagram

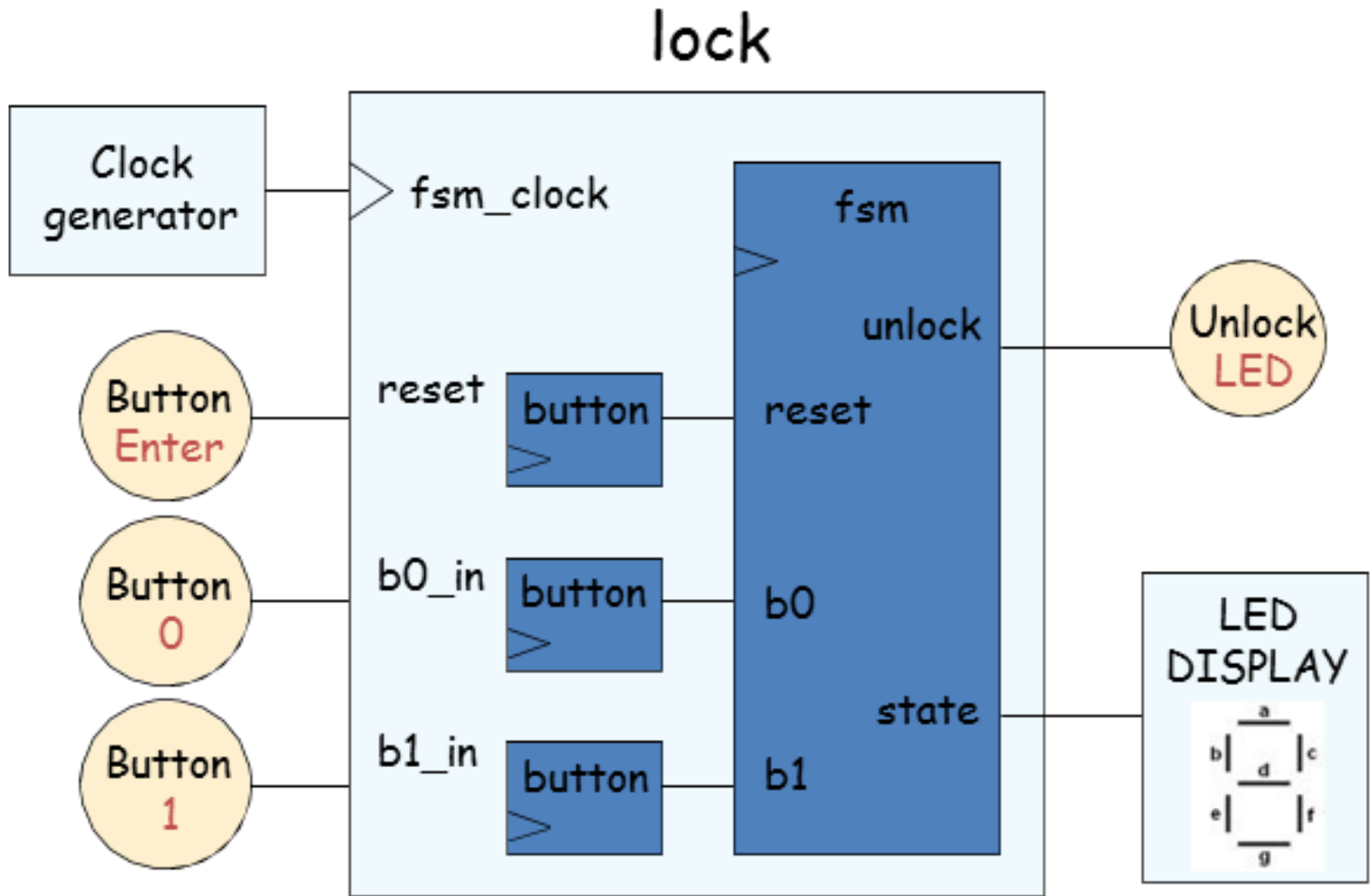


Step 1B: State transition diagram

 

Step 2. Verilog Implementation of the FSM

```
module lock(input clk, reset, b0, b1, output out);  
wire reset;  
parameter S_RESET = 0; parameter S_0= 1;           // state assignments  
parameter S_01 = 2; parameter S_010 = 3;  
parameter S_0101 = 4; parameter S_01011 = 5;  
always @(*)  
begin           // First always computes next state  
  case (state)  
    S_RESET: next_state = b0 ? S_0 : (b1 ? S_RESET : state);  
    S_0: next_state = b0 ? S_0 : (b1 ? S_01 : state);  
    S_01: next_state = b0 ? S_010 : (b1 ? S_RESET : state);  
    S_010: next_state = b0 ? S_0 : (b1 ? S_0101 : state);  
    S_0101: next_state = b0 ? S_010 : (b1 ? S_01011 : state);  
    S_01011: next_state = b0 ? S_0 : (b1 ? S_RESET : state);  
    default: next_state = S_RESET;  
  endcase  
end // always
```

 

Step 2. Verilog Implementation of the FSM

```
always @(posedge clk) // Second always computes next state
  if (reset == 1'b1)
    state <= S_RESET;
  else
    state <=next_state;

  assign out = (state == S_01011);
endmodule
```

Modeling FSMs Behaviorally

- There are many ways to do it:
 1. Define the next-state logic combinationaly and define the state-holding latches explicitly
 1. Define the behavior in a single always @posedge clk) block

Testbenches

Writing Testbenches

```
module test;  
reg a, b, sel;  
  
mux m(y, a, b, sel);  
  
initial  
begin  
    $monitor($time, "a = %b, b=%b, sel=%b, y=%b",  
             a, b, sel, y);  
    a = 0; b= 0; sel = 0;  
    #10 a = 1;  
    #10 sel = 1;  
    #10 b = 1;  
end  
endmodule
```

Inputs to device under test

Device under test (DUT)

\$monitor is a built-in event driven "printf"

Stimulus generated by sequence of assignments and delays

Writing Testbenches

```
module first_counter_tb();  
  // Declare inputs as regs and outputs as wires  
  reg clock, reset, enable;  
  wire [3:0] counter_out;  
  
  //Initialize all variables  
  initial  
    begin  
      $display ("time\t clk reset enable counter");  
      $monitor ("%g\t %b %b %b %b",  
        $time, clock, reset, enable, counter_out);  
      clock = 1; // initial value of clock  
      reset = 0; // initial value of reset  
      enable = 0; // initial value of enable  
      #5 reset = 1; // Assert the reset  
      #10 reset = 0; // De-assert the reset  
      #10 enable = 1; // Assert enable  
      #100 enable = 0; // De-assert enable  
      #5 $finish; // Terminate simulation  
    end  
  
  // Clock generator  
  always begin  
    #5 clock = ~clock; // Toggle clock every 5 ticks  
  end  
  
  // Connect DUT to test bench  
  first_counter U_counter ( clock, reset, enable, counter_out );  
  
end module
```


Simulating Verilog

Simulation Behavior

- Scheduled using an event queue
- Non-preemptive, no priorities
- A process must explicitly request a context switch
- Events at a particular time unordered
- Scheduler runs each event at the current time, possibly scheduling more as a result

Two Types of Events

- **Evaluation** events compute functions of inputs
- **Update** events change outputs
- Split necessary for delays, nonblocking assignments, etc.

Update event writes new value of a and schedules any evaluation events that are sensitive to a change on a signal

The diagram features the assignment statement $a \leq b + c$ in the center. An arrow points from the text on the left to the variable 'a' in the assignment. Another arrow points from the text on the right to the entire assignment statement.

$$a \leq b + c$$

Evaluation event reads values of b and c, adds them, and schedules an update event

Simulation Behavior

- Concurrent processes (initial, always) run until they stop at one of the following
- #42
 - Schedule process to resume 42 time units from now
- wait(cf & of)
 - Resume when expression “cf & of” becomes true
- @(a or b or y)
 - Resume when a, b, or y changes
- @(posedge clk)
 - Resume when clk changes from 0 to 1

Simulation Behavior

- Infinite loops are possible and the simulator does not check for them
- This runs forever: no context switch allowed, so ready can never change

```
while (~ready)
    count = count + 1;
```

- Instead, use

```
wait(ready);
```

Simulation Behavior

- Race conditions abound in Verilog
- These can execute in either order: final value of a undefined:

```
always @(posedge clk) a = 0;
```

```
always @(posedge clk) a = 1;
```

Verilog and Logic Synthesis

Logic Synthesis

- Verilog is used in two ways
 - Model for discrete-event simulation
 - Specification for a logic synthesis system
- Logic synthesis converts a **subset of Verilog** language into an efficient netlist
- One of the major breakthroughs in designing logic chips in the last 20 years
- Most chips are designed using at least some logic synthesis

Logic Synthesis Tools

- **Mostly commercial tools**
 - Very difficult, complicated programs to write well
 - Limited market
 - Commercial products in \$10k - \$100k price range
- **Major vendors**
 - Synopsys Design Compiler, FPGA Express
 - Cadence BuildGates
 - Synplicity (FPGAs)
 - Exemplar (FPGAs)
- **Academic tools**
 - SIS (UC Berkeley)

Logic Synthesis

- Takes place in two stages:
- Translation of Verilog (or VHDL) source to a netlist
 - Register inference
- Optimization of the resulting netlist to improve speed and area

Logic Optimization

- Netlist optimization the critical enabling technology
- Takes a slow or large netlist and transforms it into one that implements the same function more cheaply
- Typical operations
 - Constant propagation
 - Common subexpression elimination
 - Function factoring
- Time-consuming operation
 - Can take hours for large chips

Translating Verilog into Gates

- Parts of the language easy to translate
 - Structural descriptions with primitives
 - Already a netlist
 - Continuous assignment
 - Expressions turn into little datapaths
- Behavioral statements the bigger challenge

What Can Be Translated

- Structural definitions
 - Everything
- Behavioral blocks
 - Depends on sensitivity list
 - Only when they have reasonable interpretation as combinational logic, edge, or level-sensitive latches
 - Blocks sensitive to both edges of the clock, changes on unrelated signals, etc. cannot be synthesized
- User-defined primitives
 - Primitives defined with truth tables
 - Some sequential UDPs can't be translated (not latches or flip-flops)

What Isn't Translated

- **Initial blocks**
 - Used to set up initial state or describe finite testbench stimuli
 - Don't have obvious hardware component
- **Delays**
 - May be in the Verilog source, but are ignored by synthesizer
- **A variety of other obscure language features**
 - In general, things heavily dependent on discrete-event simulation semantics
 - Certain “disable” statements

Register Inference

- The main trick
- *reg* does not always equal latch
- **Rule:**
- **Combinational if outputs always depend exclusively on sensitivity list**
- **Sequential if outputs may also depend on previous values**

Register Inference

- Combinational:

```
reg y;  
always @(a or b or sel)  
  if (sel) y = a;  
  else y = b;
```

Sensitive to changes on all of the variables it reads.

Important: All outputs of the combinational circuit should be specified for every possible execution path.

y is always assigned

- Sequential:

```
reg q;  
always @(posedge clk)  
  q <= d;
```

q only assigned at posedge clk

Register Inference

- A common mistake is not completely specifying a case statement
- This implies a latch:

```
always @(a or b)
```

```
  case ({a, b})
```

```
    2'b00 : f = 0;
```

```
    2'b01 : f = 1;
```

```
    2'b10 : f = 1;
```

```
  endcase
```

f is not assigned when {a,b} = 2b'11



Register Inference

- The solution is to always have a default case

```
always @(a or b)
```

```
  case ({a, b})
```

```
    2'b00: f = 0;
```

```
    2'b01: f = 1;
```

```
    2'b10: f = 1;
```

```
    default: f = 0;
```

```
  endcase
```

f is always assigned



Inferring Latches with Reset

- Latches and Flip-flops often have reset inputs
- Can be synchronous or asynchronous
- Asynchronous positive reset:

```
always @(posedge clk or posedge reset)
  if (reset)
    q <= 0;
  else
    q <= d;
```

Inferring Latches with Reset

- Synchronous positive reset:

```
always @(posedge clk)
  if (reset)
    q <= 0;
  else
    q <= d;
```

Simulation-synthesis Mismatches

- Many possible sources of conflict
- Synthesis ignores delays (e.g., #10), but simulation behavior can be affected by them
- Simulator models X explicitly, synthesis doesn't
- Behaviors resulting from shared-variable-like behavior of regs is not synthesized
 - always `@(posedge clk) a = 1;`
 - New value of *a* may be seen by other `@(posedge clk)` statements in simulation, never in synthesis